

# UNIT 1

**Functional Blocks of a Computer:** Introduction, Block diagram of digital computer, Instruction codes, Computer Registers, Common bus system, Computer instructions, Instruction cycle and Instruction set, Register Transfer Language.

**Data Representation:** Fixed and floating point arithmetic- Addition, Subtraction, Multiplication, Division.


**Control unit Design:** Hardwired control unit, Control memory, Address sequencing, Micro-programmed control unit design, Hardwired Vs Micro-programmed design.

# Register Transfer Language (RTL)

- **Digital System:** An interconnection of **hardware modules** that do a certain task on the information.
- **Registers + Operations** performed on the data stored in them = **Digital Module**
- **Modules are interconnected** with common data and control paths to form a **digital computer system**
 
# Register Transfer Language <sup>cont.</sup>

- **Microoperations: operations executed** on data stored in one or more **registers**.
- For any function of the computer, **a sequence of microoperations** is used to describe it
- The **result of the operation** may be:
  - **replace** the previous binary information of a register or
  - **transferred** to another register



# Register Transfer Language <sup>cont.</sup>

- The **internal hardware organization** of a digital computer is defined by specifying:
  - The **set of registers** it contains and their function
  - The **sequence of microoperations** performed on the binary information stored in the registers
  - The **control that initiates** the sequence of microoperations
- **Registers + Microoperations Hardware + Control Functions = Digital Computer**

# Register Transfer Language <sup>cont.</sup>

- **Register Transfer Language (RTL)** : a **symbolic notation** to describe the microoperation transfers among registers

Next steps:


- Define **symbols** for various types of **microoperations**,
- Describe the **hardware** that implements these microoperations

# Register Transfer


- **Computer registers** are designated by **capital letters** (sometimes followed by numerals) to denote the function of the register
  - R1: processor register
  - MAR: Memory Address Register (holds an address for a memory unit)
  - PC: Program Counter
  - IR: Instruction Register
  - SR: Status Register
 
# Register Transfer <sup>cont.</sup>

- The **individual flip-flops** in an n-bit register are numbered **in sequence from 0 to n-1** (from the right position toward the left position)



Register R1

 


Showing individual bits


**A block diagram of a register**
 
# Register Transfer cont.

Other ways of drawing the block diagram of a register:



Numbering of bits

 

Partitioned into two parts



# Register Transfer cont.

- Information transfer from **one register to another** is described by a **replacement operator**:  **$R2 \leftarrow R1$** 
  - This statement denotes a transfer of the content of register R1 into register R2
- The transfer happens in **one clock cycle**
- The content of the **R1 (source) does not change**
- The content of the **R2 (destination) will be lost** and replaced by the new data transferred from R1
- We are assuming that the circuits are available from the outputs of the source register to the inputs of the destination register, and that the **destination register** has a **parallel load capability**


# Register Transfer <sup>cont.</sup>

- **Conditional transfer** occurs only under a control condition
- Representation of a (conditional) transfer  
**P:       $R2 \leftarrow R1$**
- A binary condition (**P equals to 0 or 1**) determines when the transfer occurs
- The content of **R1** is transferred into R2 only if P is 1


# Register Transfer cont.

Hardware implementation of a controlled transfer:  $P: R2 \leftarrow R1$

Block diagram:

 

Timing diagram

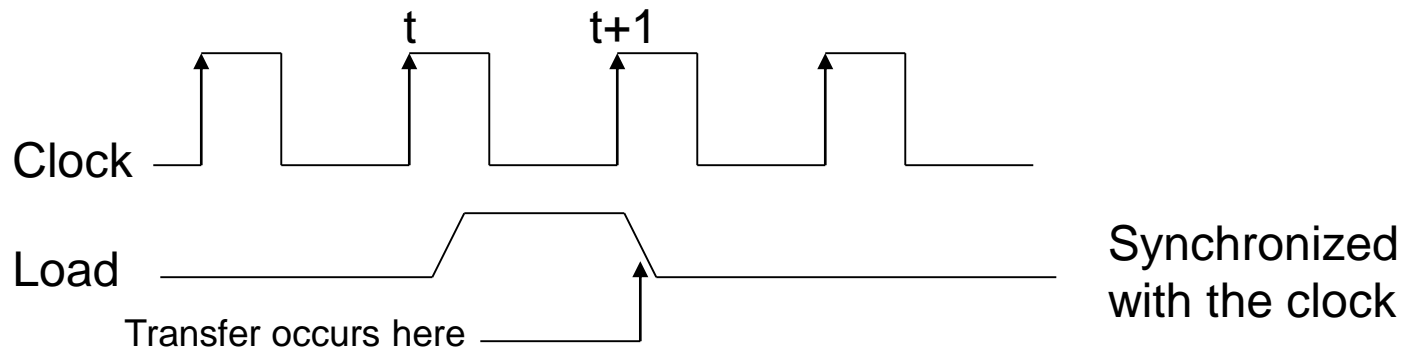

# Register Transfer cont.

Basic Symbols for Register Transfers		
Symbol	Description	Examples
Letters & numerals	Denotes a register	MAR, R2
Parenthesis ( )	Denotes a part of a register	R2(0-7), R2(L)
Arrow $\leftarrow$	Denotes transfer of information	$R2 \leftarrow R1$
Comma ,	Separates two microoperations	$R2 \leftarrow R1, R1 \leftarrow R2$

# Arithmetic Microoperations

- The **microoperations** most often encountered in digital computers are classified into **four categories**:
  - **Register transfer** microoperations
  - **Arithmetic microoperations** (on numeric data stored in the registers)
  - **Logic microoperations** (bit manipulations on non-numeric data)
  - **Shift microoperations**

# Arithmetic Microoperations <sup>cont.</sup>

- The basic **arithmetic microoperations** are: addition, subtraction, increment, decrement, and shift

- **Addition** Microoperation:

$$\mathbf{R3 \leftarrow R1 + R2}$$

- **Subtraction** Microoperation:

$$\mathbf{R3 \leftarrow R1 - R2 \text{ or :}}$$

$$\mathbf{R3 \leftarrow R1 + R2 + 1}$$

1's complement

# Arithmetic Microoperations <sup>cont.</sup>

- One's Complement Microoperation:

$$R2 \leftarrow \overline{R2}$$

- Two's Complement Microoperation:

$$R2 \leftarrow \overline{R2} + 1$$

- Increment Microoperation:

$$R2 \leftarrow R2 + 1$$

- Decrement Microoperation:


$$R2 \leftarrow R2 - 1$$

# Logic Microoperations

## The four basic microoperations

### OR Microoperation

- Symbol:  $\vee$ , +

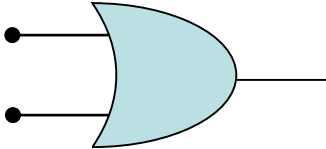- Gate: 

- Example:  $100110_2 \vee 1010110_2 = 1110110_2$

P+Q:  $R1 \leftarrow R2 + R3, R4 \leftarrow R5 \vee R6$

Diagram illustrating the OR microoperation in a register transfer statement:

- The expression  $R1 \leftarrow R2 + R3$  contains an addition operation (+), which is labeled with a callout bubble containing the word "ADD".
- The expression  $R4 \leftarrow R5 \vee R6$  contains an OR operation ( $\vee$ ), which is labeled with a callout bubble containing the word "OR".
- The overall expression is labeled with a callout bubble containing the word "OR", indicating the microoperation being performed.




# Logic Microoperations

## The four basic microoperations

cont.

### AND Microoperation

- Symbol:  $\wedge$

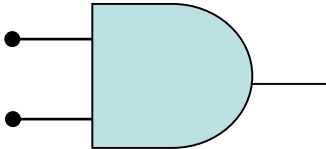- Gate: 

- Example:  $100110_2 \wedge 1010110_2 = 0000110_2$


# Logic Microoperations

## The four basic microoperations

cont.

### Complement (NOT) Microoperation

- Symbol:  $\overline{\phantom{x}}$

 

- Gate:

- Example:  $\overline{1010110_2} = 0101001_2$

# Logic Microoperations


## The four basic microoperations

cont.

### **XOR (Exclusive-OR) Microoperation**

- Symbol:  $\oplus$

- Gate:

 

- Example:  $100110_2 \oplus 1010110_2 = 1110000_2$

# Logic Microoperations


## Other Logic Microoperations

cont.

### NAND Microoperation

- Symbols:  $\wedge$  and  $\overline{\phantom{x}}$

- Gate:

 

- Example:  $100110_2 \wedge \overline{1010110_2} = 1111001_2$

# Logic Microoperations


## Other Logic Microoperations

cont.

### NOR Microoperation

- Symbols:  $\vee$  and  $\bar{\phantom{x}}$

- Gate:

 


- Example:  $100110_2 \vee 1010110_2 = 0001001_2$

# Shift Microoperations

- Used for **serial transfer of data**
- Also used in conjunction with arithmetic, logic, and other data-processing operations
- The contents of the register can be **shifted** to the **left or to the right**
- As being shifted, the **first flip-flop receives** its binary information **from the serial input**
- **Three types** of shift: **Logical, Circular, and Arithmetic**


# Shift Microoperations cont.

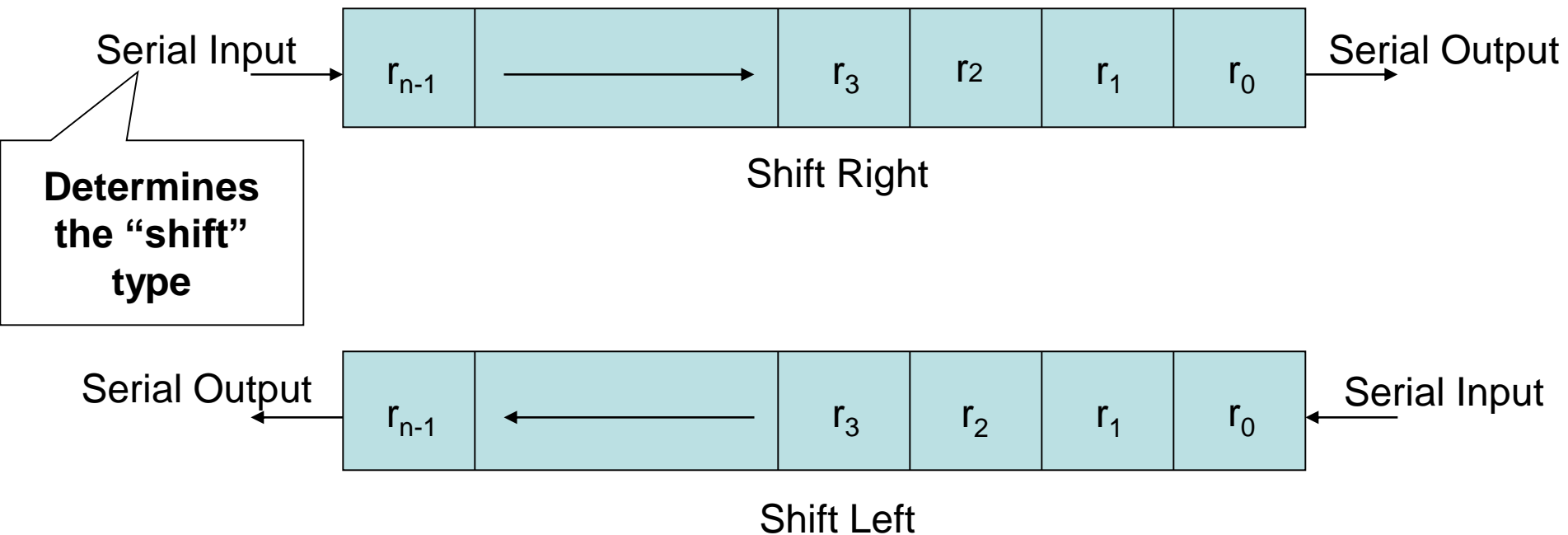

**\*\***Note that the bit  $r_i$  is the bit at position (i) of the register
 
# Shift Microoperations: Logical Shifts

- Transfers 0 through the serial input
- **Logical Shift Right:**  $R1 \leftarrow \text{shr } R1$   
The same
- **Logical Shift Left:**  $R2 \leftarrow \text{shl } R2$   
The same






# Shift Microoperations:
 
## Circular Shifts (Rotate Operation)

- Circulates the bits of the register around the two ends **without loss of information**
- **Circular Shift Right:**  $R1 \leftarrow \text{cir } R1$   
The same
- **Circular Shift Left:**  $R2 \leftarrow \text{cil } R2$   
The same



Circular Shift Left

# Shift Microoperations

## Arithmetic Shifts

- Shifts a **signed binary number** to the left or right
- An **arithmetic shift-left multiplies** a signed binary number **by 2**:    `ashl (00100): 01000`
- An **arithmetic shift-right divides** the number **by 2**  
      `ashr (00100) : 00010`
- An **overflow may occur** in **arithmetic shift-left**, and occurs when the sign bit is changed (sign reversal)


# Shift Microoperations

## Arithmetic Shifts <sup>cont.</sup>



Sign  
Bit

Arithmetic Shift Right

 

Sign  
Bit

Arithmetic Shift Left

# Shift Microoperations <sup>cont.</sup>

- Example: Assume  $R1 = 11001110$ , then:
  - Arithmetic shift right once :  $R1 = 11100111$
  - Arithmetic shift right twice :  $R1 = 11110011$
  - Arithmetic shift left once :  $R1 = 10011100$
  - Arithmetic shift left twice :  $R1 = 00111000$
  - Logical shift right once :  $R1 = 01100111$
  - Logical shift left once :  $R1 = 10011100$
  - Circular shift right once :  $R1 = 01100111$
  - Circular shift left once :  $R1 = 10011101$